

# Circuits for sensors

---

Ideal OP Amps

Basic OP Amp Circuit Blocks

Analog Computation

Nonlinear OP Amp Applications

OP Amp Considerations

Guarding


Passive Filters

Active Filters

VCO(Voltage Controlled Oscillator)
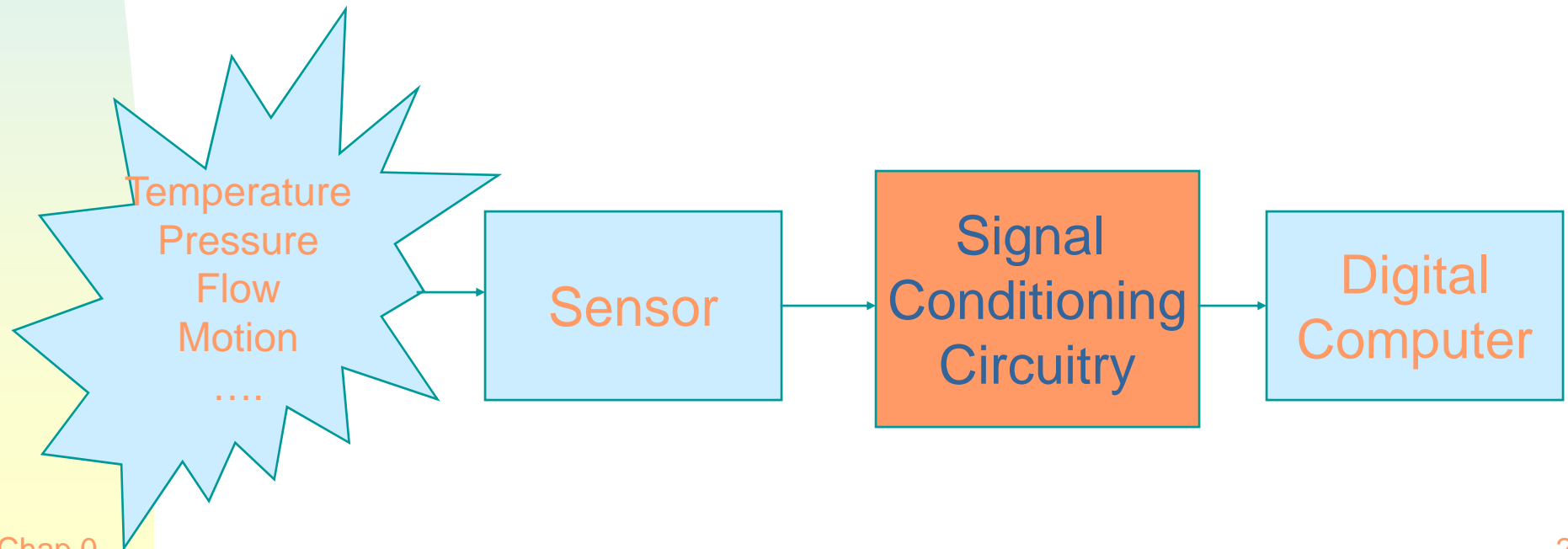
# Function of Amplifiers

- **Amplifiers provides**
  - ◆ GAIN
  - ◆ Filtering, Signal processing, Correction for Nonlinearities



# Ideal OP Amps

- **Transfer Function = Output / Input**


- ◆ Voltage Amp TF (Gain):  $A_v = \frac{v_o}{v_i}$

- ◆ Usually  $A_v \geq 1$

- ◆ OP Amp is preferred

- ☞ Easy to use in circuit designed compared to discrete Transistor circuits

# Ideal OP Amps (Cont.)

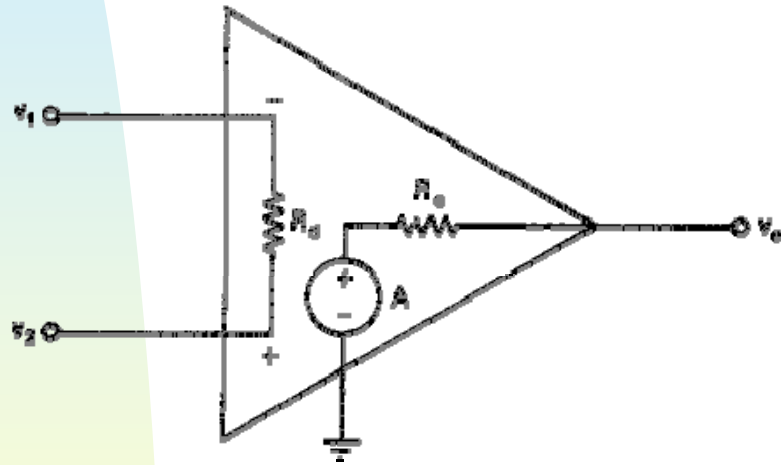

## ■ Assumptions

- ◆ Open loop Gain = Infinity
- ◆ Input Impedance  $R_d = \text{Infinity}$
- ◆ Output Impedance  $R_o = 0$
- ◆ Bandwidth = Infinity
  - ☞ Infinite Frequency Response
- ◆  $v_o = 0$  when  $v_1 = v_2$ 
  - ☞ No Offset Voltage

# Ideal OP Amps (Cont.)

## ■ Note

◆  $v_0 = A(v_2 - v_1)$

☞ If  $v_0 = \infty$ ,  $A = \infty$  (Typically 100,000)

• Then  $v_2 - v_1 = 0 \Rightarrow v_2 = v_1$

☞ Since  $v_2 = v_1$  and  $R_d = \infty$

• We can neglect the current in  $R_d$

## ■ Rule 1

◆ When the OP Amp is in linear range the two inputs are at the same voltage

## ■ Rule 2


◆ No Current flows into either terminal of the OP Amp

# Basic OP Amp Circuit Blocks

- **Inverting Amplifier**
- **Noninverting Amplifier**
- **Unity-Gain Amplifier**
- **Differential Amplifier**
- **Instrumental Amplifier**
- **The Electrocardiogram Amplifier**
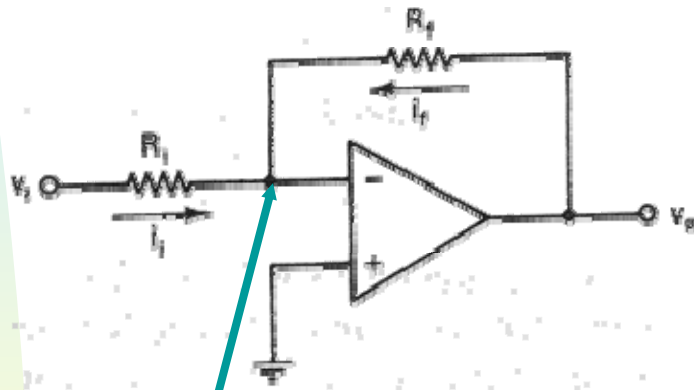
# Inverting Amplifier

- Inverting Amp with Gain =  $-R_f / R_i$




Virtual Ground

- From Rule 1
  - ◆  $v_- = v_+ = 0$
- From Rule 2 & KCL
  - ◆  $i_i + i_f = 0 \Rightarrow i_i = -i_f$
  - ◆ From Ohm's law
    - ☞  $i_i = v_i / R_i$ ,  $i_f = v_o / R_f$
  - ◆  $v_i / R_i = -v_o / R_f$ 
    - ☞  $v_o / v_i = -R_f / R_i$
- Inverting Amp Gain
  - ◆  $-R_f / R_i$

# Inverting Amplifier (Cont.)

- **Linear Range**

- ◆ By Power Supply Voltage

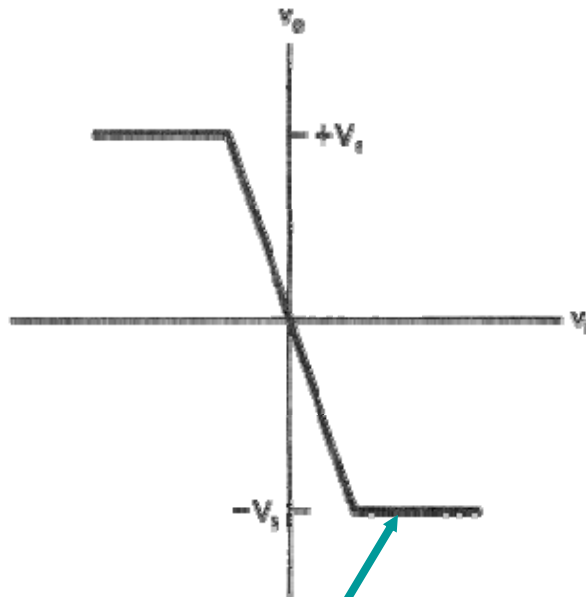

**Saturation**

- **Input Impedance**


- ◆ Low ( $R_i$ )
- ◆ Increasing  $R_i \rightarrow$  Decreasing Gain
  - ☞ Increasing Gain by increasing  $R_f$ 
    - But there is practical limit



# Noninverting Amplifiers

- **Noninverting Amp**

- ◆ Gain =  $(R_f + R_i) / R_f$

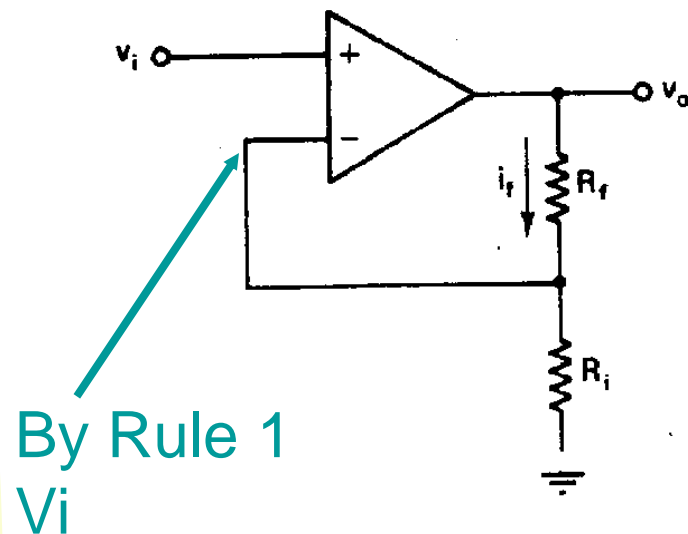

- **By Rule 2**

- ◆  $V_o = I_f \times (R_f + R_i)$

- ◆  $V_i = I_f \times R_i$

- ◆  $V_o = V_i \times (R_f + R_i) / R_i$

- **Gain:  $V_o / V_i = 1 + R_f / R_i$**


- **Gain  $\geq 1$ , Always**

- **Input Impedance**

- ◆ Very Large (Infinite)
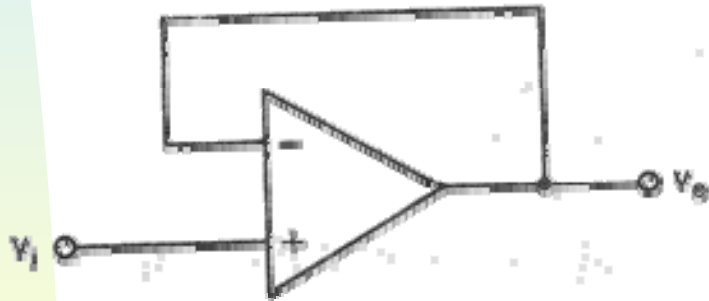
# Unity-Gain Amplifier


- ◆ Verify that the Gain of Unity-Gain Amp is 1



- **$V_o = V_i$**
- **Applications**
  - ◆ Buffer amplifier
    - ☞ Isolate one circuit from the loading effects of a following stage
  - ◆ Impedance converter
    - ☞ Data conversion System (ADC or DAC) where constant impedance or high impedance is required
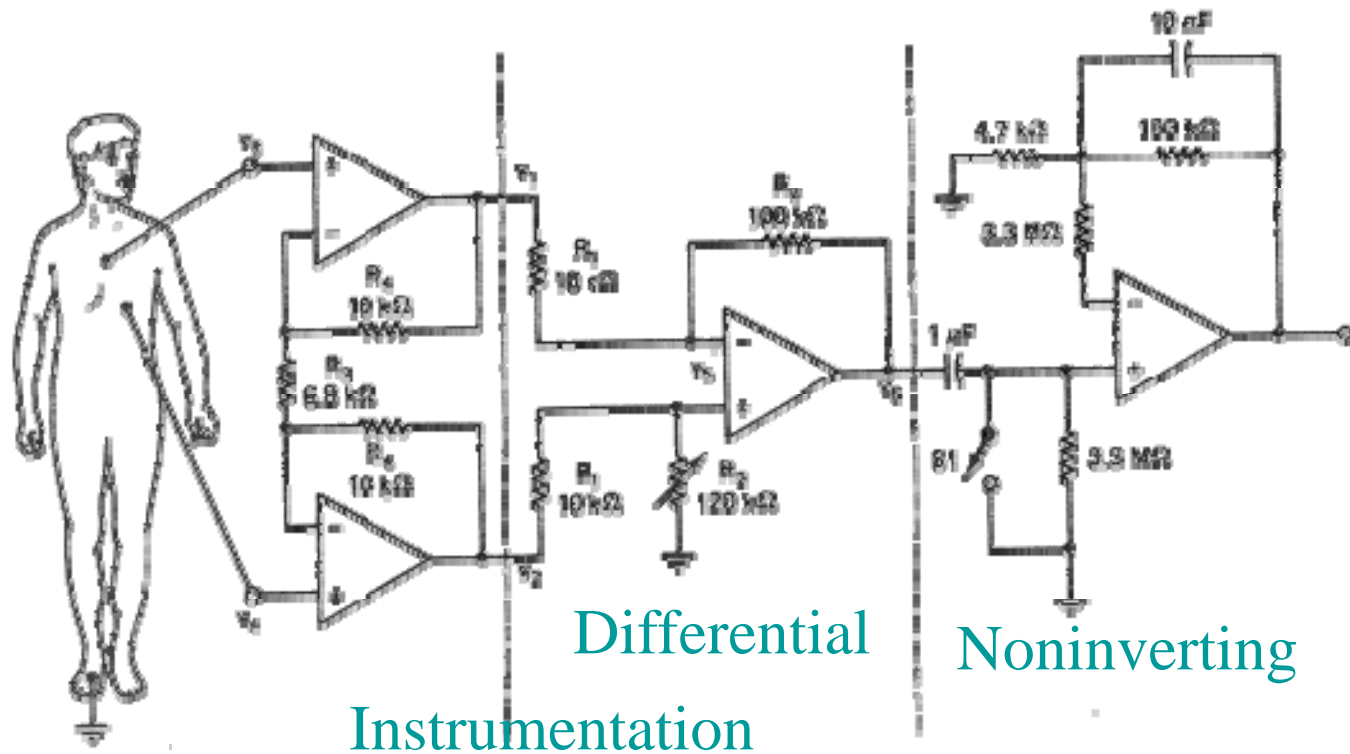
# Differential Amplifiers

- Combination of Inverting and Noninverting Amp
- Can reject 60Hz interference
- Electrocardiogram amplifier



# Differential Amplifiers (Cont.)

## ■ Gain of Differential Amp

### ◆ By Rule 2

☞  $V_5 = I_2 * R_2$

☞  $V_2 = I_2 * R_1 + V_5 = V_5 * R_1 / R_2 + V_5$


☞  $V_5 = R_2 * V_2 / (R_1 + R_2)$

### ◆ By Rule 1

☞  $V_1 = R_1 * I_1 + V_5$

☞  $V_5 = R_2 * I_1 + V_6$

☞  $V_6 = (V_2 - V_1) * R_2 / R_1$

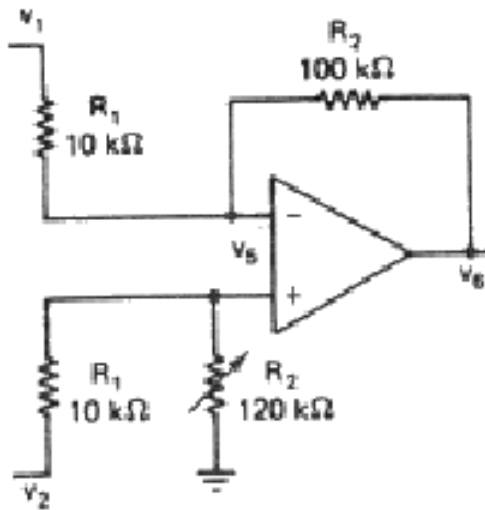

# Differential Amplifiers (Cont.)

- **CMV (Common Mode Voltage)**
  - ◆ If  $V_1 = V_2$ , then  $V_6 = 0$
- **CMG (Common Mode Gain) = 0**
- **DG(Differential voltage Gain)**
  - ◆ If  $V_1 \neq V_2$ , then  $V_6 = (V_2 - V_1) * (R_2 / R_1)$
- **In practice, CMG  $\neq 0$**
- **CMRR (Common Mode Rejection Ratio)**
  - ◆ Measure of the ability to reject CMV
  - ◆  $CMRR = DG / CMG$ 
    - ☞ The Higher CMRR, the better quality
    - ☞ Typically, 100 ~ 10,000
    - ☞ 60Hz noise common to  $V_1$  and  $V_2$  can be rejected

# Instrumentation Amplifiers

- **One OP Amp Differential Amplifier**

- ◆ Input Impedance is not so High

- ☞ Good for Low impedance source

- Strain gage Bridge

- ☞ Bad for High impedance source


- **Instrumentation Amplifier**

- ◆ Differential Amp with High Input Impedance and Low Output Impedance

- ◆ Two Noninverting Amp + One Differential Amp
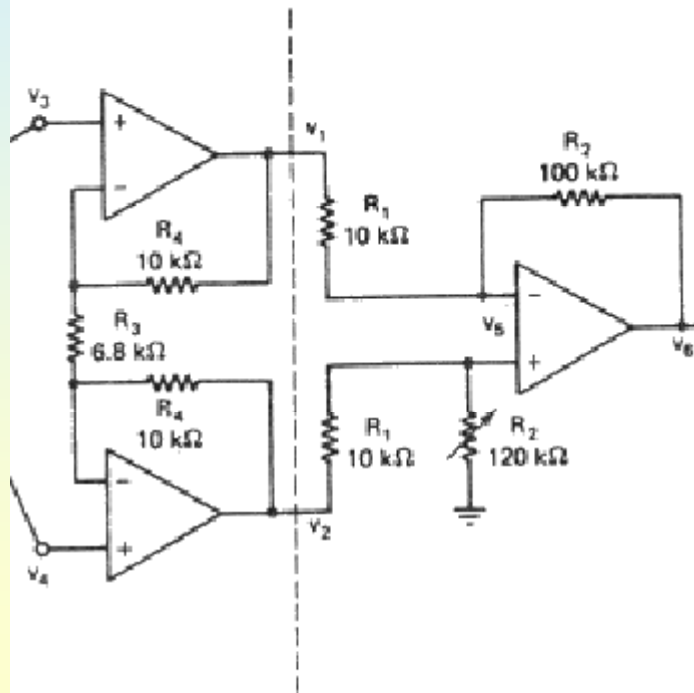
# Instrumentation Amplifiers (Cont.)

- Instrumentation Amp = Noninverting Amp + Differential Amp




- ◆ We have:

$$\begin{aligned} \Rightarrow DG &= (V1-V2) / (V3-V4) \\ &= (2 \cdot R4 + R3) / R3 \end{aligned}$$

$$\Rightarrow V6 = (V3-V4) \cdot DG \cdot R2 / R1$$

- First Stage CMRR
  - ◆  $CMRR = DG / CMG = DG$
- Overall CMG = 0
  - ◆ High CMRR
- High Input Impedance
- Gain is adjustable by changing R3

# The Electrocardiogram Amplifier

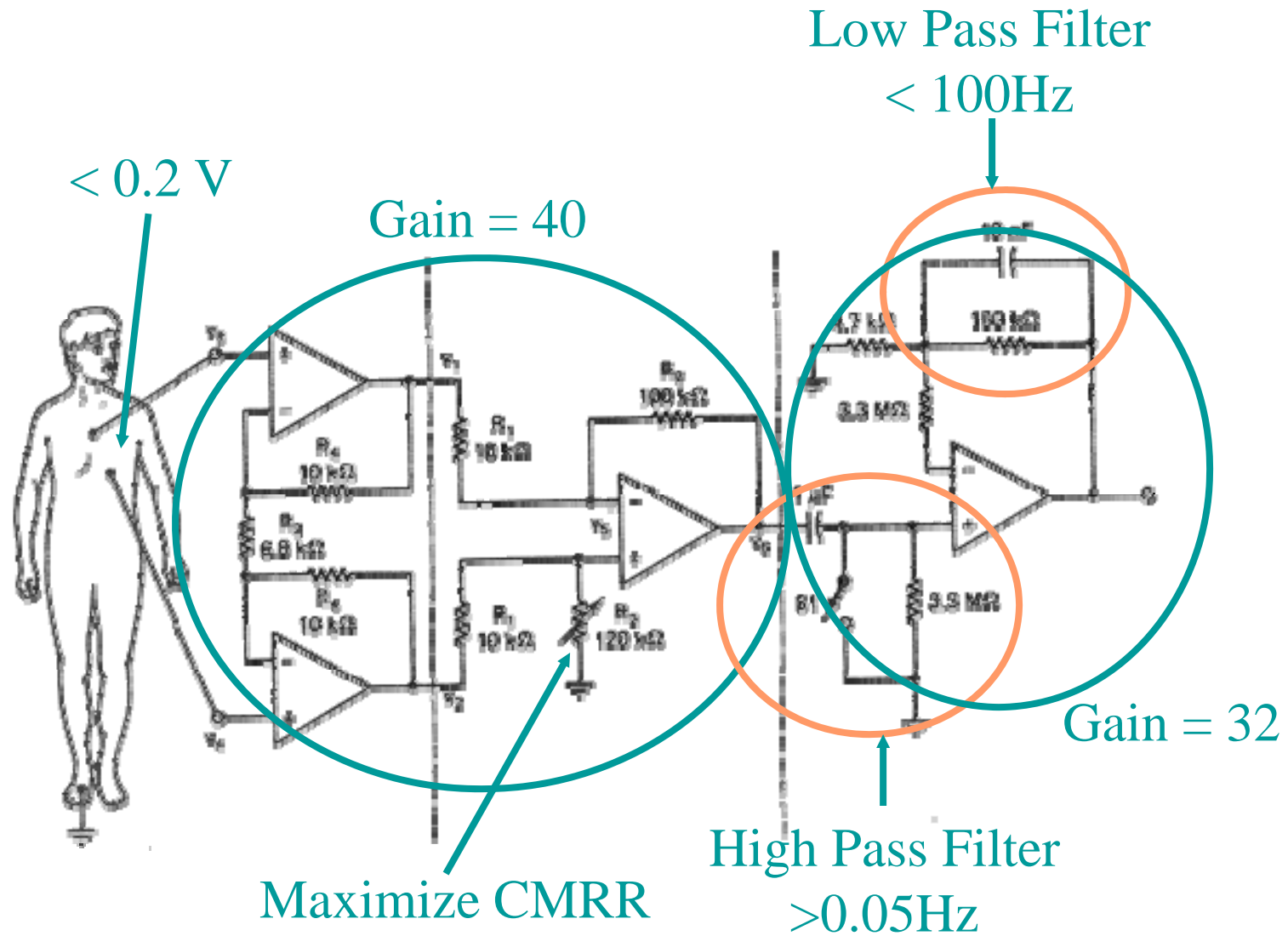




# Analog Computation

- **Digital Signal Processing is preferred**
  - ◆ Flexibility
  - ◆ Easy to Change
  - ◆ Elimination of hardware
- **Analog Signal Processing**
  - ◆ Is preferred when DSP consumes too much time
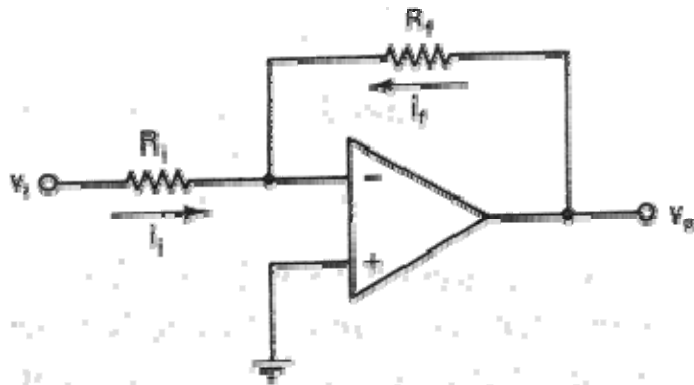
# Inverter and Scale Changer

- **Inverting Amp with Gain = - Rf / Ri**




- **Inverter**
  - ◆  $R_f / R_i = 1$
- **Inverter and Scale Changer**
  - ◆ Proper choice of  $R_f / R_i$
- **Application**
  - ◆ Use of inverter to scale the output of DAC

# Adders (Summing Amplifiers)

- **Adder**


- ◆ Inverter with Several inputs

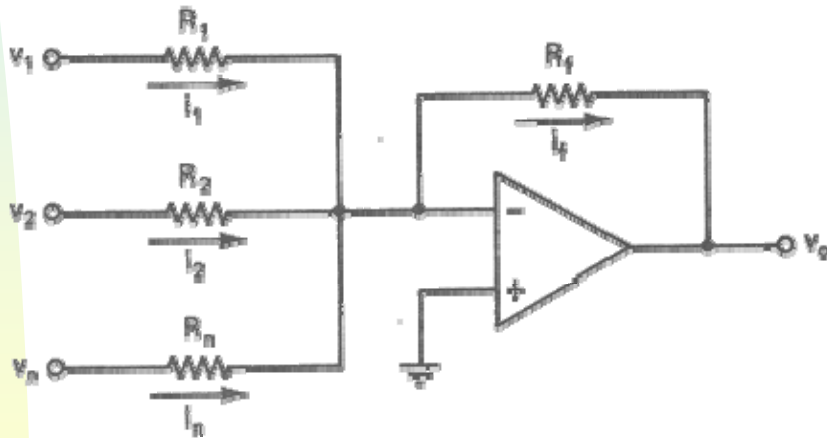

- $V_o = -R_f(V_1/R_1 + V_2/R_2 + \dots + V_n/R_n)$ 
  - ◆  $I_f = I_1 + I_2 + I_n$
  - ◆  $I_1 = V_1/R_1, \dots$
  - ◆  $V_o = -I_f * R_f$
- **R<sub>f</sub> determines overall Gain**
- **R<sub>i</sub> determines weighting factor and input impedance**
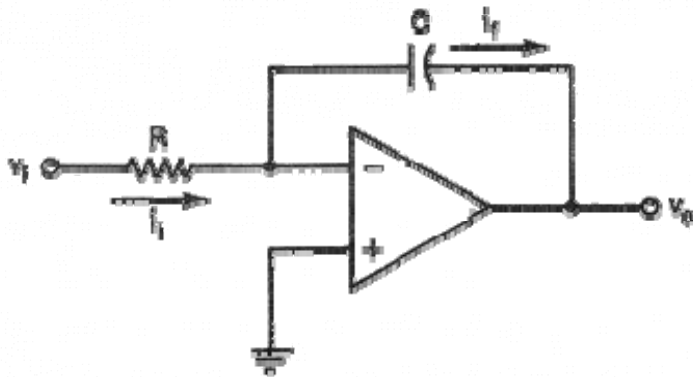
# Integrator


$$v_o = \frac{-1}{RC} \int_0^{t_1} v_i dt + v_{ic}$$




- **Drawbacks**

- ◆  $V_o$  will reach saturation voltage, if  $V_i$  is left connected indefinitely
  - ☞ Integrator operates as an open-loop amplifier for DC inputs

# Practical Integrator

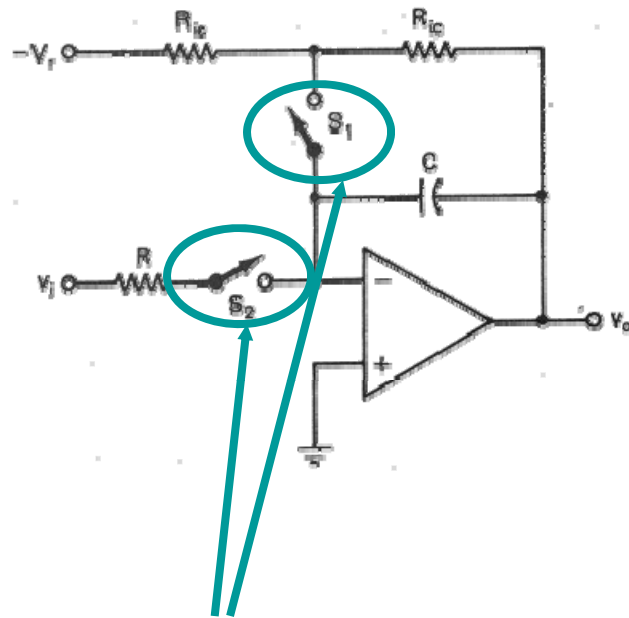

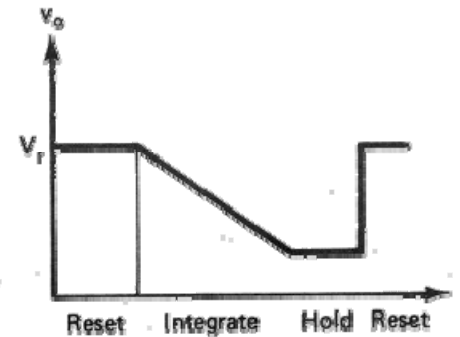
Controlled By  
Relay or  
Solid State Switch or  
Analog Switch



- **Reset**
  - ◆ **S1 Closed, S0 Open**
    - ☞ Inverter
    - ☞ C is initialized to  $V_r$
- **Integrate**
  - ◆ **S1 Open, S0 Closed**
- **Hold**
  - ◆ **S1 Open, S0 Open**
  - ◆ **Keeps  $V_o$  constant**
    - ☞ Read and Process

# Differentiators

$$v_o = -RC \frac{dv_i}{dt}$$

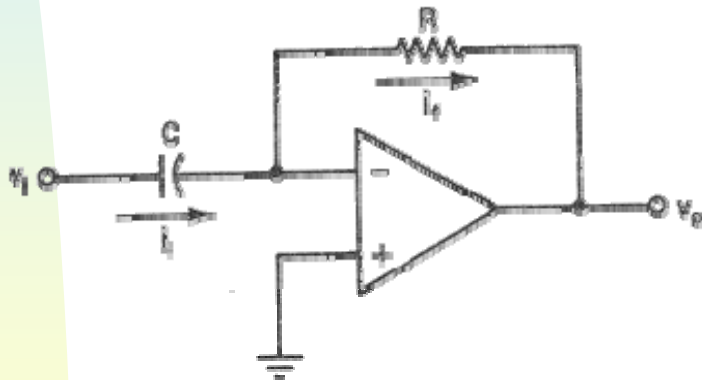


- **Drawbacks**

- ◆ Instability at High frequencies

- **Practical Differentiator**

- ◆ To Stable
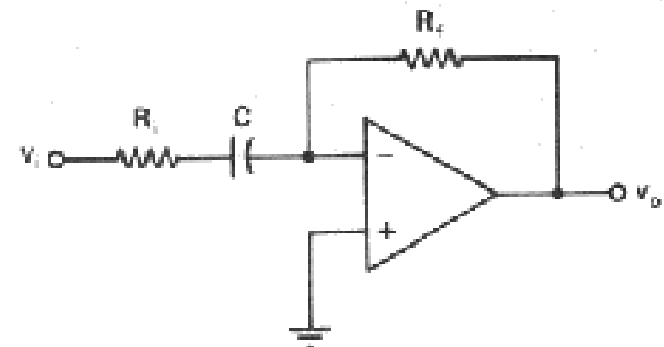
$$R_i = \sqrt{\frac{R}{A_0 \omega_0 C}}$$



# Comparators


- **Compare Two Inputs**

- ◆  $V_i > V_r$

- ☞  $V_o = -V_s$

- ◆  $V_i < V_r$


- ☞  $V_o = V_s$

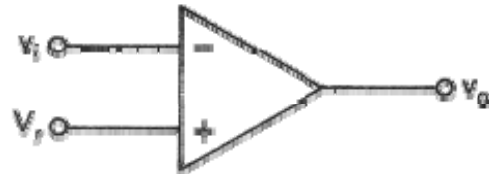

- **Drawbacks**


- ◆ If  $V_i = V_r + \text{small noise}$

- ☞ Rapid fluctuation between  $\pm V_s$

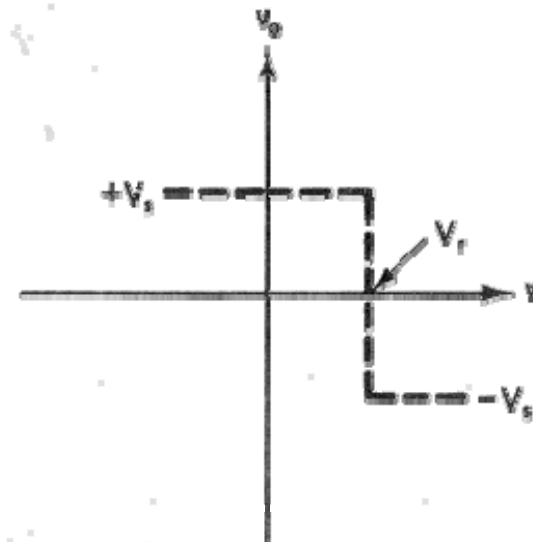

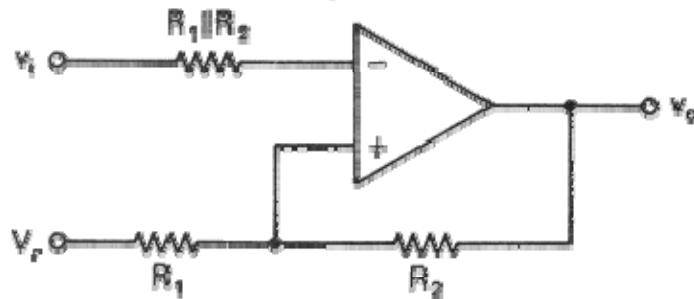
# Comparators with Hysteresis

- **Positive Feedback**
  - ◆ Hysteresis loop
  - ◆ Can remove the effect of Small Noise
    - Reduce Fluctuation



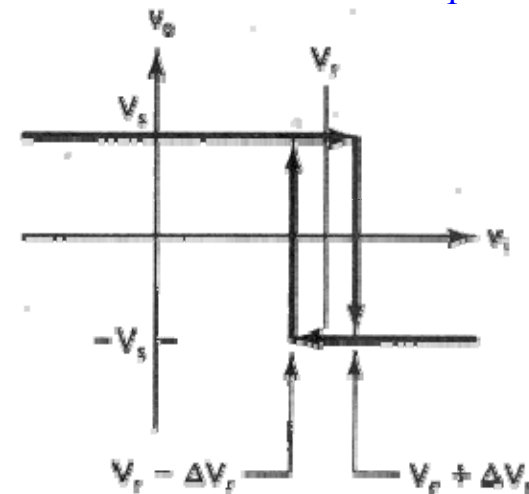
$$V_r + \Delta V_r = V_r + \frac{(V_S - V_r)R_1}{R_1 + R_2}$$
$$V_r - \Delta V_r = V_r + \frac{(-V_S - V_r)R_1}{R_1 + R_2}$$






# Rectifiers


- Precision Half Wave Rectifier

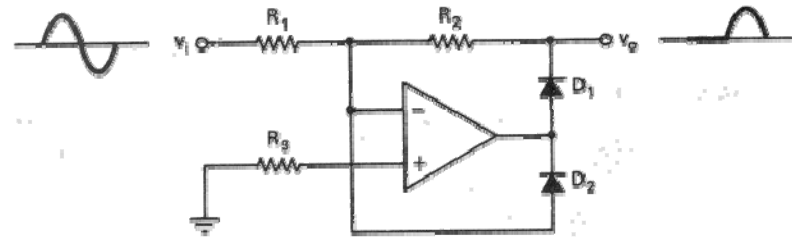

- Precision Full Wave Rectifier

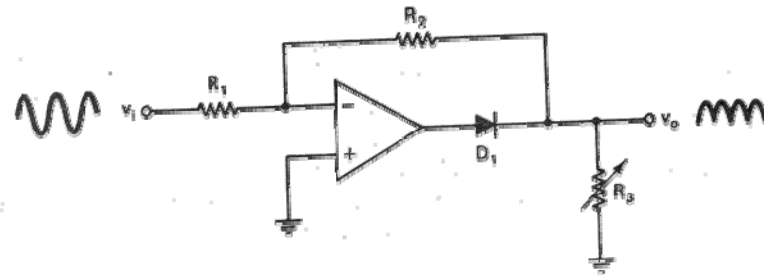

- Limiters

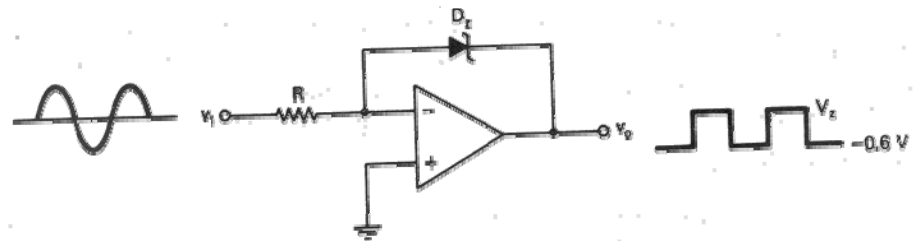

# OP Amp Considerations

- **Effects of Nonlinear characteristics**
  - ◆ Compensation
    - ☞ Undesirable Oscillation at High frequency
      - Add external Capacitance according to Spec sheet
  - ◆ GBW (Gain Bandwidth Product)
    - ☞  $\text{Gain} \times \text{Bandwidth} = \text{Constant}$  (Typically 1MHz)
      - For Noninverting Amp:  $\text{Bandwidth} = \text{GBW} / \text{Gain}$
  - ◆ Input Offset Voltage
    - ☞ Practical OP Amp
      - Zero input Does NOT give Zero output
    - ☞ Input Offset Voltage
      - Applied input voltage to obtain Zero output
    - ☞ Nulling the offset Voltage
      - Adding External Resister according to Spec sheet

# OP Amp Considerations (Cont.)

## ◆ Input Bias Current

### ☞ Practical OP amp

- Current flowing into the terminal is NOT Zero
- To keep the input Tr of OP amp turned on
- Causes errors proportional to feedback network R

### ☞ To minimize errors

- feedback R should be low ( $<10\text{K}\Omega$ )

## ◆ Slew Rate

### ☞ Maximal rate of change of amplifier output voltage

- Ex: Slew rate of 741 =  $0.5\text{ V} / \mu\text{s}$ 
  - Time to output change from  $-5\text{V}$  to  $5\text{V}$  =  $20\ \mu\text{s}$

### ☞ To Minimize slew rate problem

- Use OP amp with smaller external compensating C

# OP Amp Considerations (Cont.)

## ◆ Power Supply

- ☞ Usually  $\pm 15V$ 
  - Linear Range  $\pm 13V$
- ☞ Reducing power supply voltage
  - Results reduced linear range
  - Device does not work  $< 4V$

## ◆ Different OP Amps

- ☞ Bipolar Op Amps
  - Good input offset stability
  - Moderate input bias current and Input resistances
- ☞ FET
  - Very Low input bias current and Very High Input resistances
  - Poor Input offset voltage stability

# Guarding

- **Elimination of Surface Leakage Currents**
- **Elimination of Common Mode Signals**
  
- **Very important in practice**
  - ◆ But skip in this course

# Passive Filters

## ■ Passive Circuits

- ◆ Contains only passive elements
  - ☞ Registers, Capacitors and Inductors
- ◆ Examples
  - ☞ Bridge Circuit
  - ☞ Voltage Divider
  - ☞ Filters

## ■ Filters



- ◆ Eliminate unwanted signal from the loop
- ◆ Low Pass, High Pass, Band Pass, Notch, ...

# Passive first-order Low pass Filter

- Pass desired Audio signal and reject undesired RF
- Order of Filter
  - ◆ Number of C and L

$$\frac{V_o}{V_i} = \frac{1}{1 + j\omega\tau}, \quad \tau = RC$$

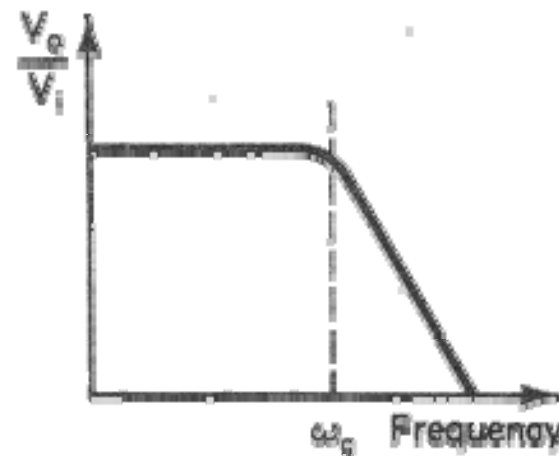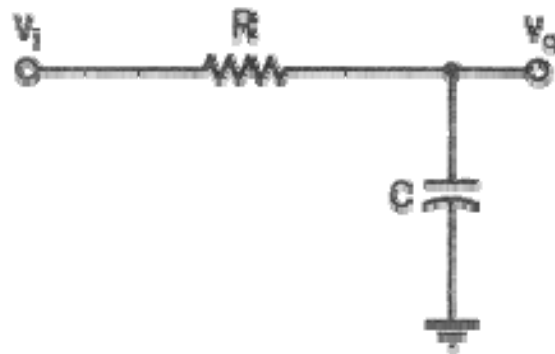- ◆ Plot Magnitude and Phase plot (Bode plot)
- ◆ Meaning of  $\omega_C$





# Passive first-order High pass Filter

- Pass desired High frequency signal and reject undesired low frequency signal

$$\frac{V_o}{V_i} = \frac{j\omega\tau}{1 + j\omega\tau}, \quad \tau = RC$$

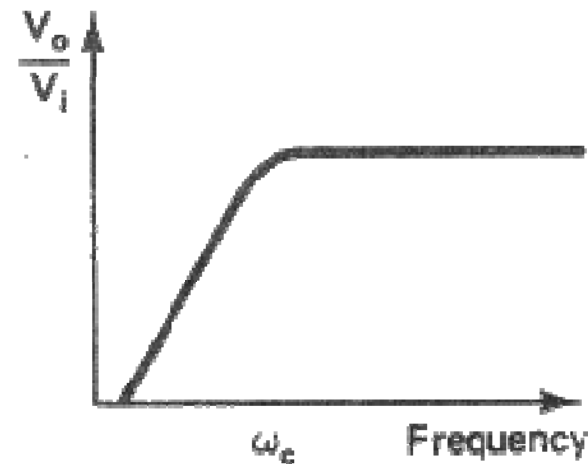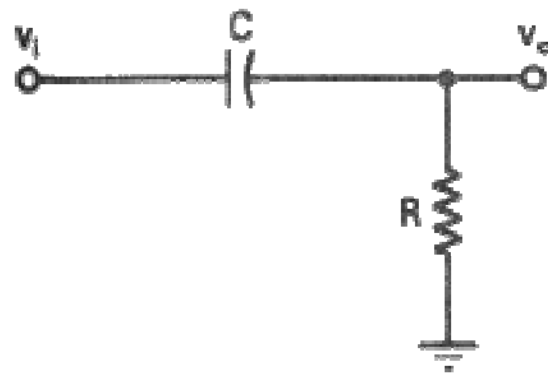- ◆ Plot Magnitude and Phase plot (Bode plot)
- ◆ Meaning of  $\omega_c$





# Passive second-order Low pass Filter



- To increase the attenuation of transfer function
- Order of Filter
  - ◆ Number of C and L

$$\frac{V_o}{V_i} = \frac{1}{(j\omega/\omega_c)^2 + (2\zeta j\omega/\omega_c) + 1}$$

$$\omega_c = \sqrt{\frac{1}{LC}}, \zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

- ◆ Meaning of Quality factor

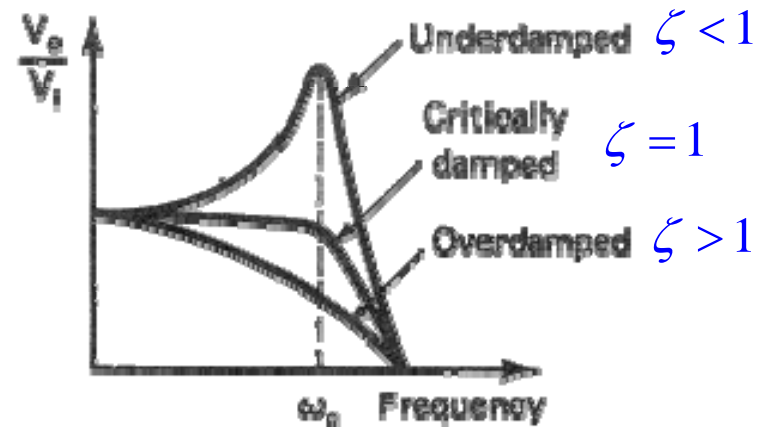
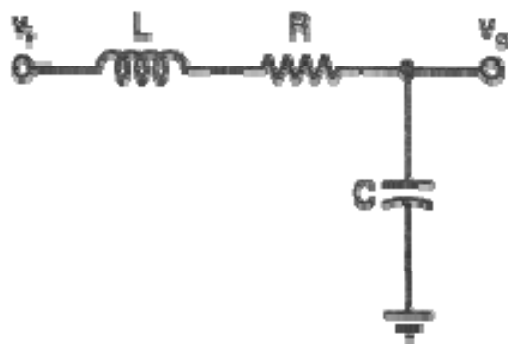
$$Q = \frac{1}{2\zeta} = \frac{\omega_c}{\Delta\omega}, \Delta\omega = 3dB BW$$


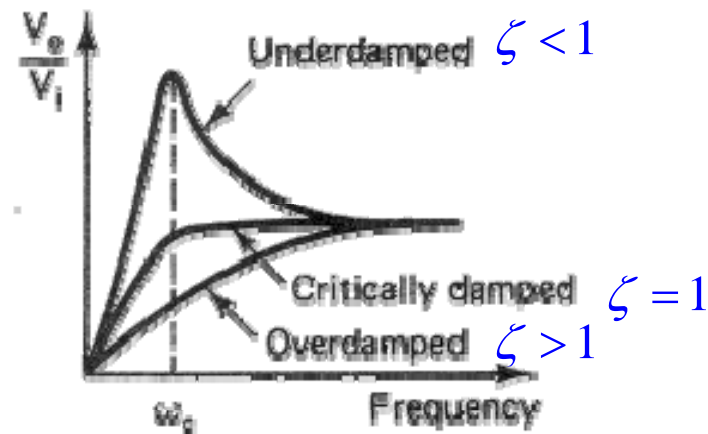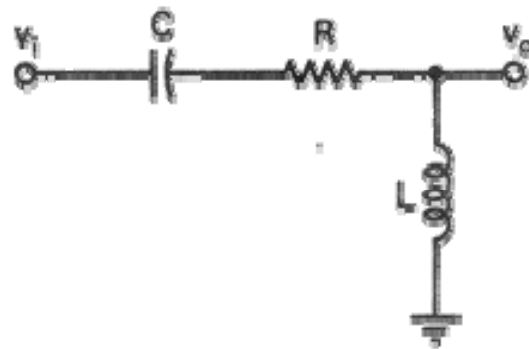
# Passive second-order High pass Filter



- To increase the attenuation of transfer function
- Order of Filter
  - ◆ Number of C and L

$$\frac{V_o}{V_i} = \frac{\omega^2}{(j\omega/\omega_c)^2 + (2\zeta j\omega/\omega_c) + 1}$$
$$\omega_c = \sqrt{\frac{1}{LC}}, \zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$



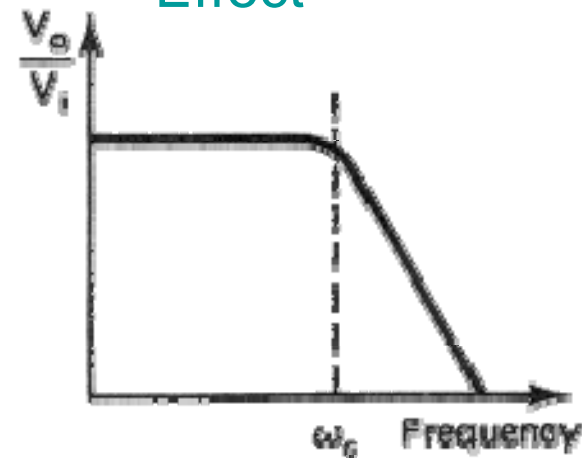
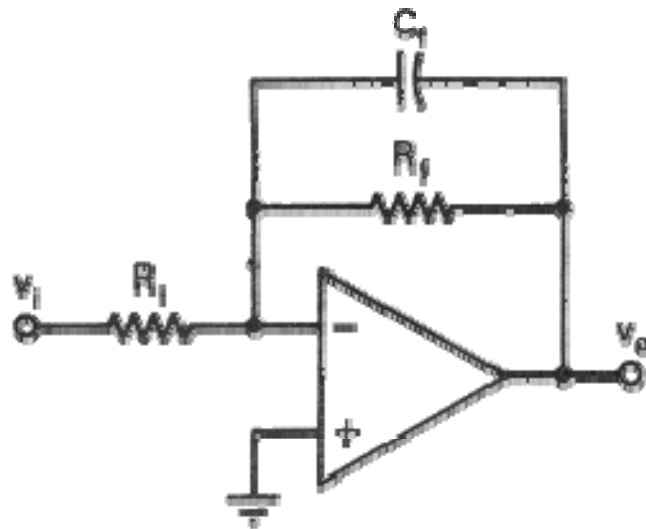
# Active First-order Low Pass Filter

- Inverting Amp + Feedback Capacitor
- Identical frequency response with Passive filter
- Very Low Output impedance
  - ◆ Negligible Loading Effect



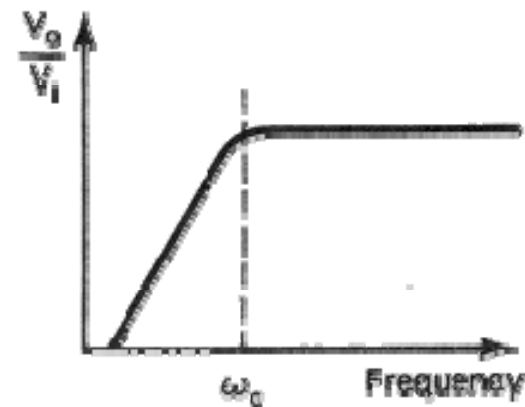
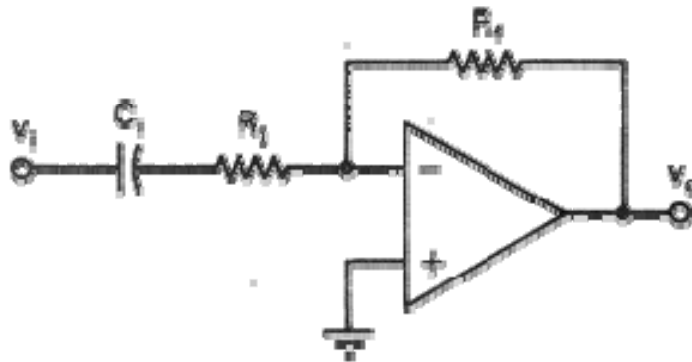
# Active First-order High Pass Filter

- Inverting Amp + Input Capacitor
- Identical frequency response with Passive filter
- Very Low Output impedance
  - ◆ Negligible Loading Effect





# Active High-order Filters

- Low Pass Filters

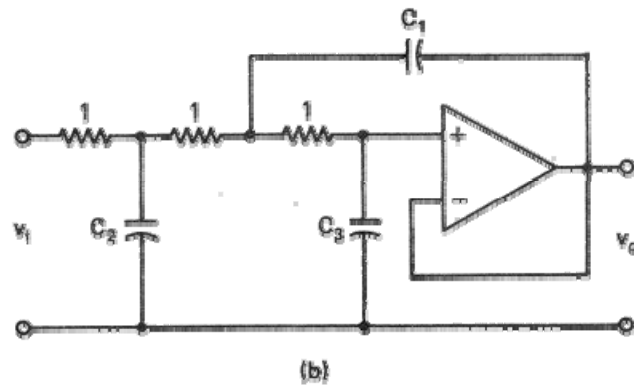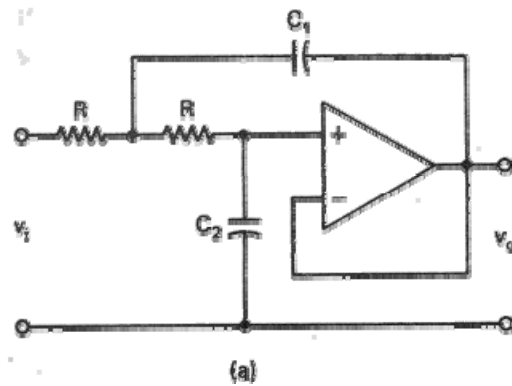

- High Pass Filters

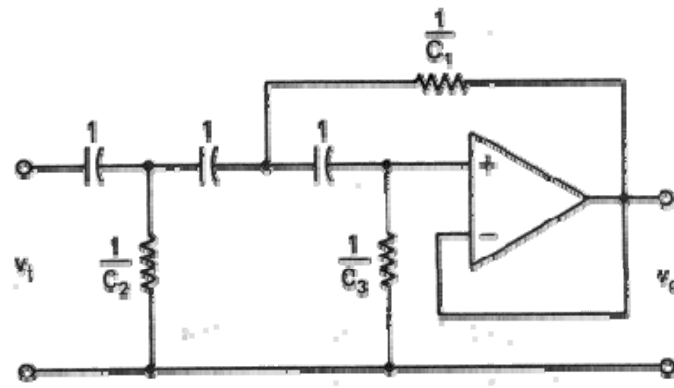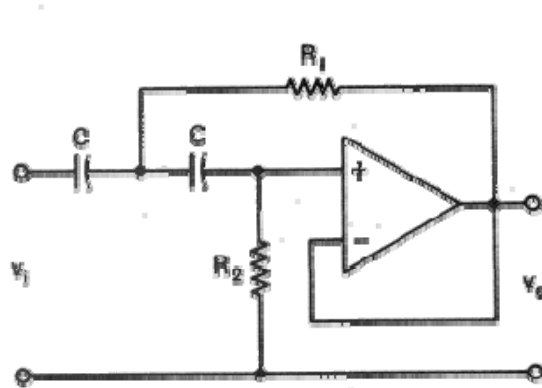

# Bandpass and Band-reject Filters

- **Butterworth Filters**
  - ◆ Maximally Flat Magnitude response in pass band
  - ◆ High Attenuation Rate
- **Chebyshev Filters**
  - ◆ Maximum Attenuation Rate
  - ◆ Ripple in pass band
- **Bessel Filters**
  - ◆ Maximally flat time delay in response to step input
  - ◆ Attenuation Rate is very gradual


# Filter Design Table

- C when  $\omega_0 = R_0 = 1$

Poles	C <sub>1</sub>	C <sub>2</sub>	C <sub>3</sub>	C <sub>1</sub>	C <sub>2</sub>	C <sub>3</sub>
	Bessel			Butterworth		
2	9.066 -1	6.799 -1		1.414 +0	7.071 -1	
3	1.423 +0	9.880 -1	2.538 -1	3.546 +0	1.392 +0	2.024 -1
4	7.351 -1	6.746 -1		1.082 +0	9.241 -1	
	1.012 +0	3.900 -1		2.613 +0	3.825 -1	
5	1.009 +0	8.712 -1	3.095 -1	1.753 +0	1.354 +0	4.214 -1
	1.041 +0	3.098 -1		3.235 +0	3.089 -1	
6	6.352 -1	6.098 -1		1.035 +0	9.660 -1	
	7.225 -1	4.835 -1		1.414 +0	7.071 -1	
	1.073 +0	2.561 -1		3.863 +0	2.588 -1	
	2-dB Chebyshev			0.25-dB Chebyshev		
2	2.672 +0	5.246 -1		1.778 +0	6.789 -1	
3	2.782 +1	3.113 +0	3.892 -2	8.551 +0	2.018 +0	1.109 -1
4	4.021 +0	1.163 +0		2.221 +0	1.285 +0	
	9.707 +0	1.150 -1		5.363 +0	2.084 -1	
5	1.240 +1	4.953 +0	1.963 -1	5.543 +0	2.898 +0	3.425 -1
	1.499 +1	7.169 -2		8.061 +0	1.341 -1	
6	5.750 +0	1.769 +0		3.044 +0	1.875 +0	
	7.853 +0	2.426 -1		4.159 +0	4.296 -1	
	2.146 +1	4.902 -2		1.136 +1	9.323 -2	
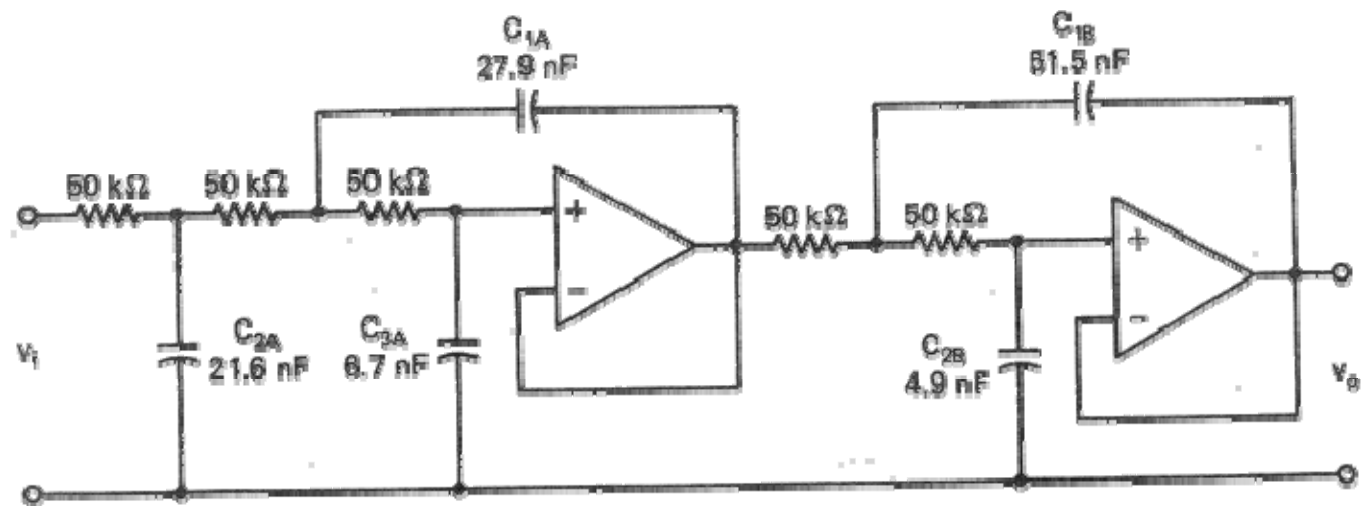
# Filter Design Example


- **Low pass five-pole Butterworth filter with a corner frequency of 200Hz and input resistance of 50K $\Omega$** 
  - ◆ Economic Solution = 3<sup>rd</sup> order + 2<sup>nd</sup> order
  - ◆ Desired R and C ?
    - ☞  $C_{1A} = (\omega_0 R_0 C_0) / (\omega R)$   
 $= 1 \times 1 \times 1.753 / 2\pi \times 200 \times 50K = 27.9 \text{ nF}$
    - ☞  $C_{2A} = 21.6 \text{ nF}$ ,  $C_{3A} = 6.7 \text{ nF}$ ,  $C_{1B} = 51.5 \text{ nF}$ ,  $C_{2B} = 4.9 \text{ nF}$




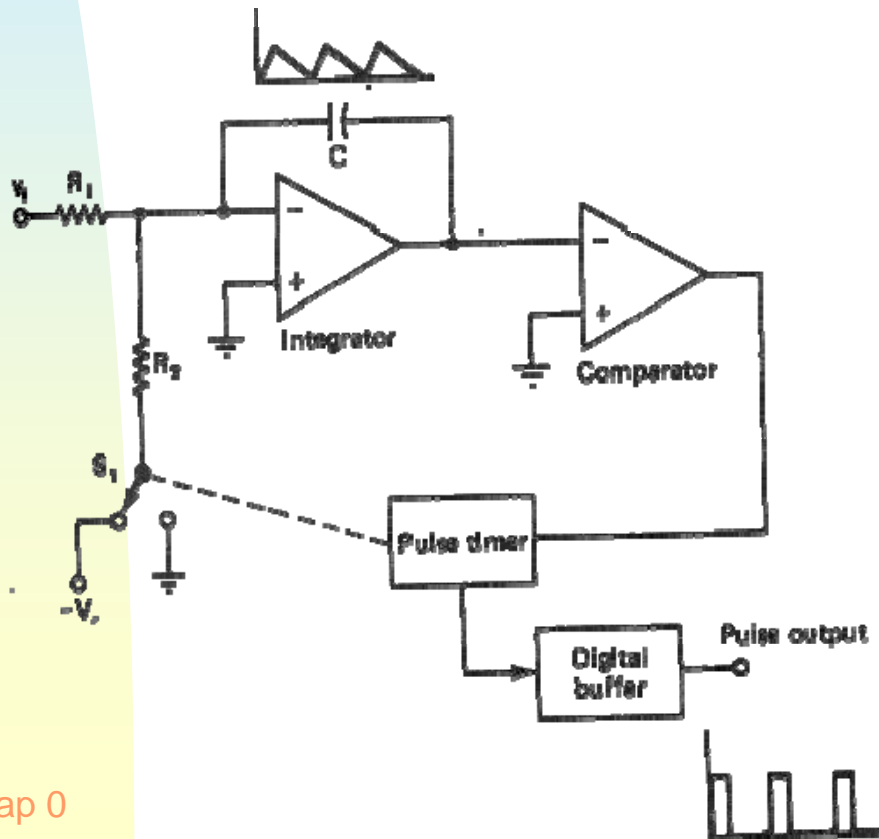
# VCO(Voltage Controlled Oscillator)

- VCO = Voltage to Frequency(V/F) Converter




- VCO converts an input voltage to a series of output digital pulses whose frequency is proportional to the input voltage
- Applications
  - ◆ ADC
  - ◆ Digital Transmission
  - ◆ Telemetry
  - ◆ Digital Voltmeter

# VCO (Cont.)

- **Module form**
  - ◆ Better linearity, Lower Gain drift, Higher full-scale frequencies than IC
- **Monolithic IC form**
  - ◆ Less expensive, Small size
  - ◆ Lower drift, Better flexibility of frequency range
- **Examples**
  - ◆ LM331
    - ☞ Low cost VCO from National Semiconductor
    - ☞ Maximum nonlinearity 0.01% over 1 ~ 100KHz
  - ◆ CD4046B
    - ☞ PLL contains VCO
    - ☞ Maximum nonlinearity 1.0% over 1 ~ 400MHz
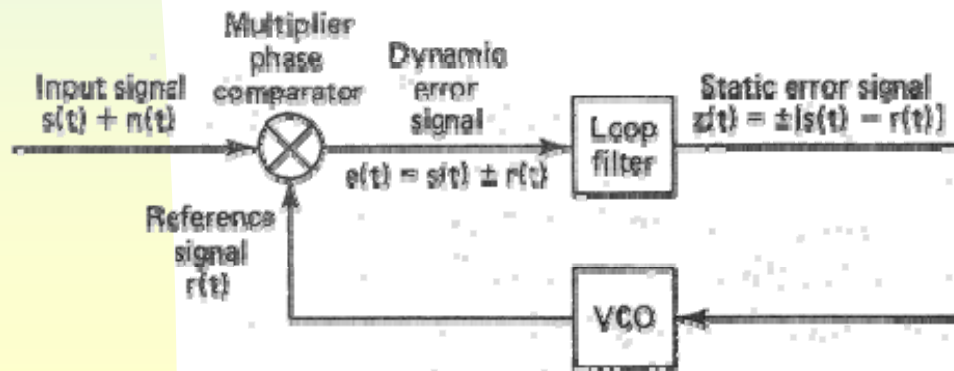
# PLL(Phase Locked Loop)

- VCO is commonly used in PLL
- Applications
  - ◆ Communications
  - ◆ Radar
  - ◆ Time and frequency control
  - ◆ Instrumentation system
- Control loop
  - ◆ Goal
    - ☞ Minimize  $z(t)$   
→  $s(t) = r(t)$
  - ◆ Change  $r(t)$  until  $z(t)=0$ 
    - ☞  $s(t)$  can be obtained  
By reading  $r(t)$



# VCO Interfacing

- **Output of VCO**

- ◆ Digital pulses whose frequency is proportional to input voltage


- **# of pulse / Duration**

- ◆ Duration

- ☞ Controlled by Sampling Gate

- ◆ # of Pulse


- ☞ Counted in Counter

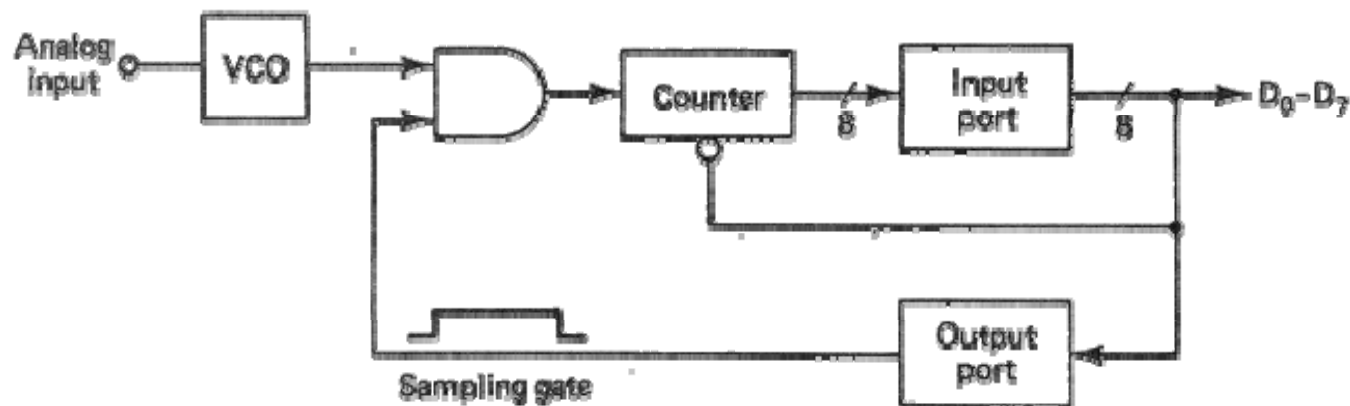
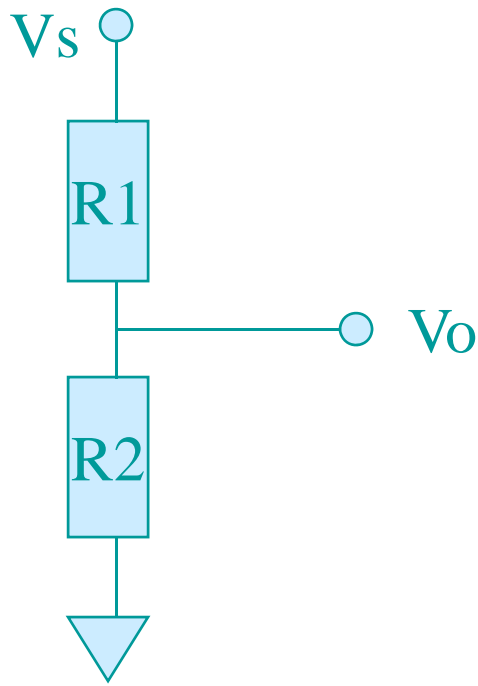
# Divider Circuit


- **Convert Register Variations to Voltage Variations**

- **Output Voltage**
  - ◆  $V_o = \{R_2 / (R_1 + R_2)\} V_s$


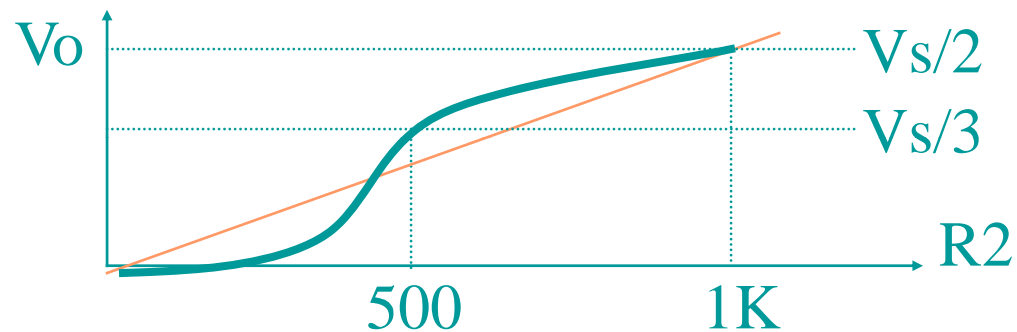
# Divider Circuit: Drawbacks

- **$V_o$  is not linearly changed**
  - ◆ Ex:  $V_s = 5V$ ,  $R_1 = 1K\Omega$ ,  $R_2 = 0 \sim 1K\Omega$ (Sensor)



- **Output Impedance( $R_1 \parallel R_2$ ) is not so High**
- **Large Power Consumption**

# Divider Circuit: Example

- **$R1 = 10K\Omega$ ,  $R2 = (4K \sim 12K\Omega)$ ,  $Vs = 5V$** 
  - ◆ Maximum  $V_o = 5 \{12 / (10+12)\} = 2.73V$
  - ◆ Minimum  $V_o = 5 \{4 / (10 + 4)\} = 1.43V$
  - ◆ Maximum  $Z = (10K \parallel 12K) = 120/22 K\Omega$
  - ◆ Minimum  $Z = (10K \parallel 4K) = 40/14 K\Omega$
  - ◆ Maximum Power =  $(V_o)^2/R2$   
 $= (2.73)^2/12K = 0.62mW$
  - ◆ Minimum Power =  $(1.43)^2/4K = 0.51mW$